

Department of Electronics & Communication Engineering

Faculty of Engineering, Integral University, Lucknow

Home Assignment-3

Basic Electrical Engineering (IEN-101)

Faculty : Dr. Syed Hasan Saeed

Section : EC-1

Problems : 05

1. State various parts of a transformer and their functions.
2. Explain the working principle of a transformer.
3. The primary winding of a transformer has 300 turns. When connected across a 220V, 50Hz supply, it draws a current of 5 A at a power factor of 0.25 on no-load. Determine (a) the maximum value of core flux (b) magnetizing current and (c) the loss in the core. How many turns are required in the secondary to step-up the voltage to 415V?
[3.03mW, 4.84A, 275W, 566]
4. Write short notes on core losses.
5. The open circuit and short circuit test on a 4-kVA, 200/400V, 50Hz, single phase transformer gave the following result
OC test on LV side: 200V, 1 A, 100 W
SC test with LV side shorted: 15 V, 10 A, 85 W
Determine the parameters of the equivalent circuit and draw the equivalent circuit referred to the LV side.

[0.2125 Ω , j0.309 Ω , 0.0025S, 0.0433S]